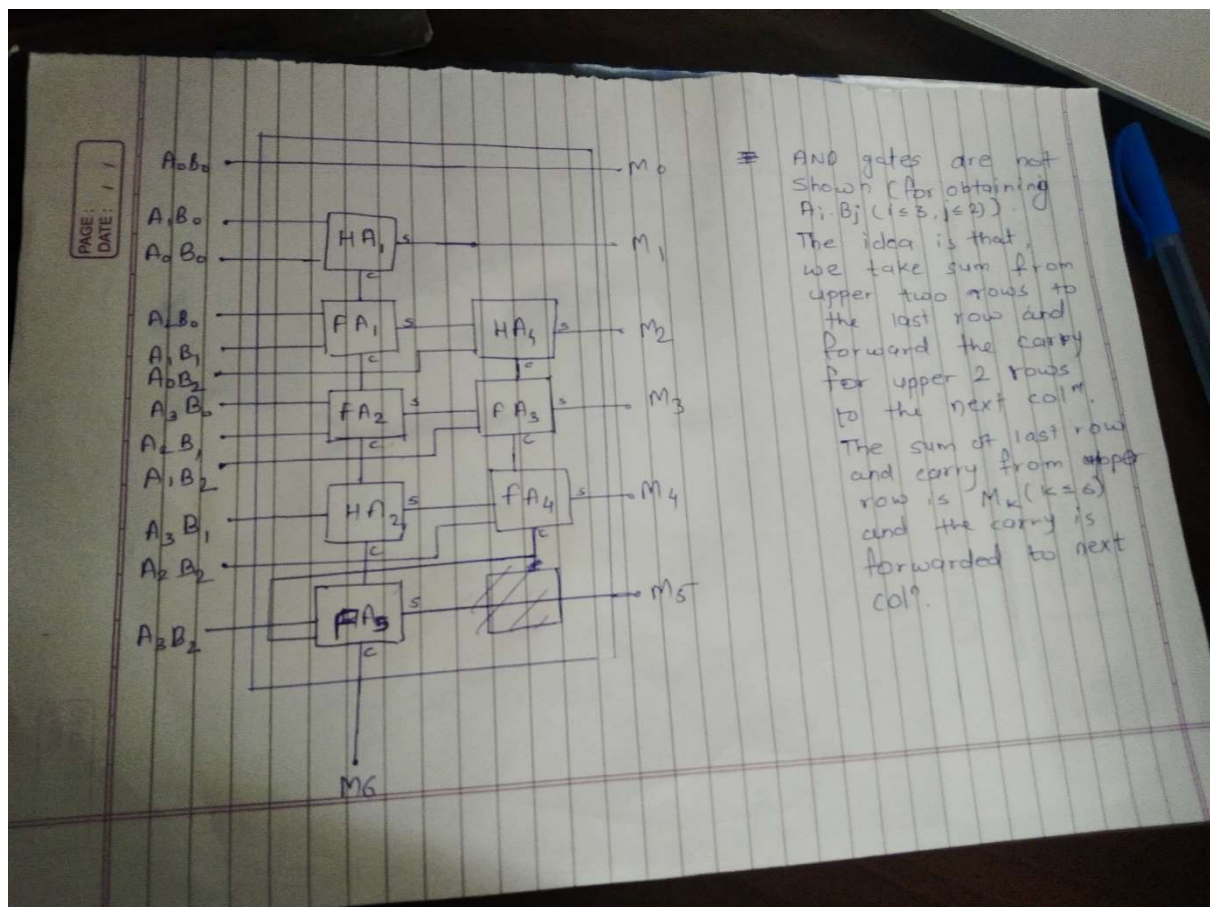


EXP_03 : 4 bit by 3 bit MULTIPLIER

In this lab, we designed a 4bit by 3bit Multiplier , which multiplies a 4 bit binary no. by a 3 bit binary no. .

Design includes 12 AND gates(for product terms) , 4 Half Adders and 5 Full Adders .



VHDL desc for Multiplier is :

```
entity Multiplier_4x1 is
    port (B2,B1,B0,A3,A2,A1,A0: in std_logic;
          Y6,Y5,Y4,Y3,Y2,Y1,Y0 : out std_logic);
end entity Multiplier_4x1;

architecture Struct of Multiplier_4x1 is
    signal S11,S10,S9,S8,S7,S6,S5,S4,S3,S2,S1,t10,t9,t8,t7,t6,t5,t4,t3,t2,t1: std_logic;
begin
    -- component instances

    N1 : AND_2 port map(A=>A0,B=>B0,Y=>Y0);
    N2 : AND_2 port map(A=>A1,B=>B0,Y=>S1);
    N3 : AND_2 port map(A=>A2,B=>B0,Y=>S2);
    N4 : AND_2 port map(A=>A3,B=>B0,Y=>S3);
    N5 : AND_2 port map(A=>A0,B=>B1,Y=>S4);
    N6 : AND_2 port map(A=>A1,B=>B1,Y=>S5);
    N7 : AND_2 port map(A=>A2,B=>B1,Y=>S6);
    N8 : AND_2 port map(A=>A3,B=>B1,Y=>S7);
```

```

N9 : AND_2 port map(A=>A0,B=>B2,Y=>S8);
N10 :AND_2 port map(A=>A1,B=>B2,Y=>S9);
N11 :AND_2 port map(A=>A2,B=>B2,Y=>S10);
N12 :AND_2 port map(A=>A3,B=>B2,Y=>S11);
HA1 : HALF_ADDER port map(A=>S1,B=>S4,S=>Y1,C=>t1);
FA1 : FULL_ADDER port map(A=>S2,B=>S5,Cin=>t1,S=>t2,C=>t3);
HA2 : HALF_ADDER port map(A=>t2,B=>S8,S=>Y2,C=>t4);
FA2 : FULL_ADDER port map(A=>S3,B=>S6,Cin=>t3,S=>t5,C=>t6);
FA3 : FULL_ADDER port map(A=>t5,B=>S9,Cin=>t4,S=>Y3,C=>t7);
HA4 : HALF_ADDER port map(A=>S7,B=>t6,S=>t8,C=>t9);
FA4 : FULL_ADDER port map(A=>S10,B=>t8,Cin=>t7,S=>Y4,C=>t10);
FA5 : FULL_ADDER port map(A=>S11,B=>t9,Cin=>t10,S=>Y5,C=>Y6);
end Struct;

```

Input and Output format of DUT:

Input MSB = A3

Input LSB = B0

Output MSB = Y6

Output LSB = Y0

Input-Output format in Tracefile :-

<A3 A2 A1 A0 B2 B1 B0> <Y6 Y5 Y4 Y3 Y2 Y1 Y0>

Testcases from TRACEFILE :-

```

0000000 0000000 1111111
0000001 0000000 1111111
0000010 0000000 1111111


```

```


0000011 0000000 1111111
0000100 0000000 1111111
0000101 0000000 1111111
0000110 0000000 1111111
0000111 0000000 1111111
0001000 0000000 1111111
0001001 0000001 1111111
0001010 0000010 1111111
0001011 0000011 1111111
0001100 0000100 1111111
0001101 0000101 1111111
0001110 0000110 1111111
0001111 0000111 1111111
0010000 0000000 1111111
0010001 0000010 1111111
0010010 0000100 1111111
0010011 0000110 1111111

```


RTL View of Multiplier :

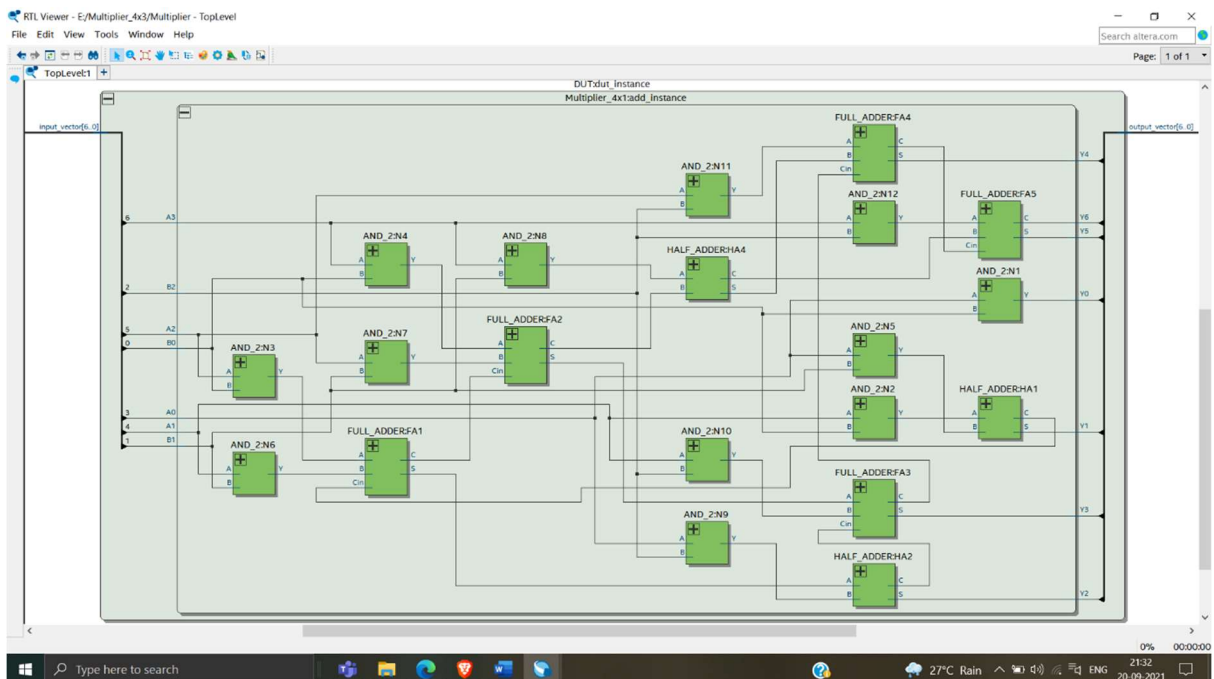

RTL Simulation :

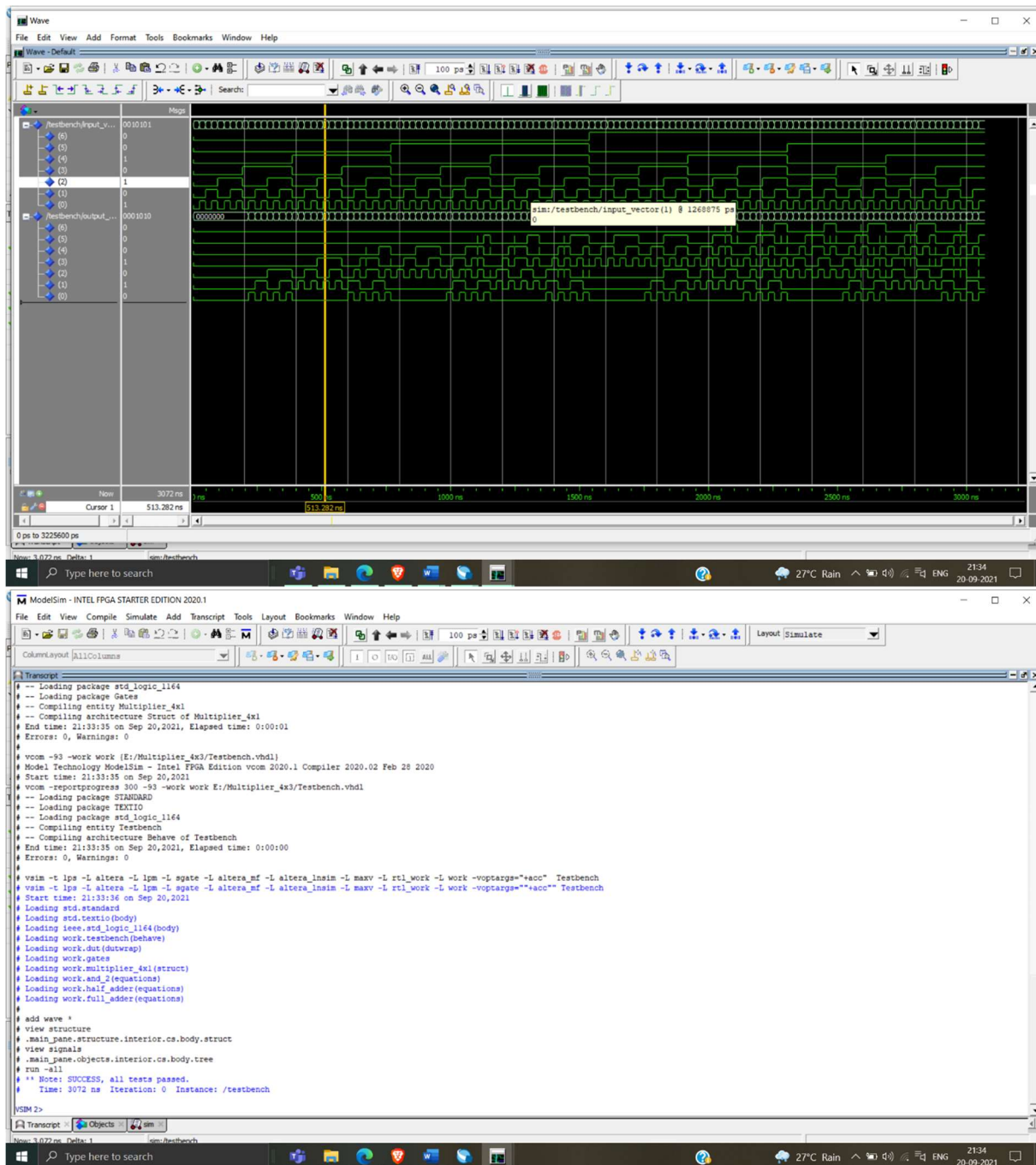


GATE level Simulation:

 

```
ModelSim - INTEL FPGA STARTER EDITION 2020.1
File Edit View Compile Simulate Add Transcript Tools Layout Bookmarks Window Help
ColumnLayout [allColumns]
Transcript
-- Loading package std_logic_1164
-- Loading package Gates
-- Compiling entity Multiplier_4x1
-- Compiling architecture Struct of Multiplier_4x1
End time: 21:41:01 on Sep 20, 2021, Elapsed time: 0:00:00
Errors: 0, Warnings: 0
vcom -93 -work work [E:/Multiplier_4x3/Testbench.vhdl]
Model Technology ModelSim - Intel FPGA Edition vcom 2020.1 Compiler 2020.02 Feb 28 2020
Start time: 21:41:01 on Sep 20, 2021
vcom -reportprogress 300 -93 -work work E:/Multiplier_4x3/Testbench.vhdl
-- Loading package STANDARD
-- Loading package TEXTIO
-- Loading package std_logic_1164
-- Compiling entity Testbench
-- Compiling architecture Behave of Testbench
End time: 21:41:01 on Sep 20, 2021, Elapsed time: 0:00:00
Errors: 0, Warnings: 0
vsim -t lps -l altera -l lpm -l sgate -l altera_mf -l altera_lnsim -l maxv -l rtl_work -l work -voptargs="" -acc Testbench
vsim -t lps -l altera -l lpm -l sgate -l altera_mf -l altera_lnsim -l maxv -l rtl_work -l work -voptargs="" -acc Testbench
Start time: 21:41:01 on Sep 20, 2021
Loading std.standard
Loading std.textio(body)
Loading ieee.std_logic_1164(body)
Loading work.testbench(behave)
Loading work.dot(dotwrap)
Loading work.gates
Loading work.multiplier_4x1(struct)
Loading work.and_2(equations)
Loading work.half_adder(equations)
Loading work.full_adder(equations)
add wave *
view structure
.main_panel.structure.interior.cs.body.structure
view signals
.main_panel.objects.interior.cs.body.tree
run -all
** Note: SUCCESS, all tests passed.
Time: 3072 ns Iteration: 0 Instance: /testbench
NSIM 2>
```


Testing on Scanchain:

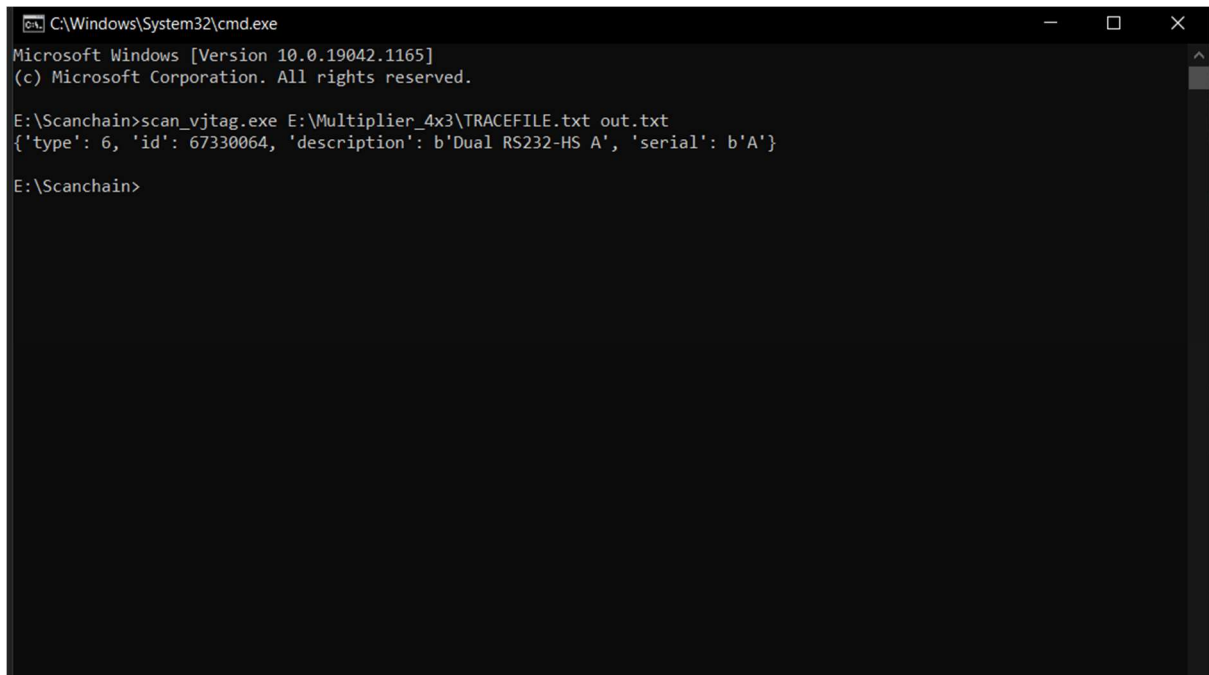

```
C:\Windows\System32\cmd.exe
Microsoft Windows [Version 10.0.19042.1165]
(c) Microsoft Corporation. All rights reserved.

E:\Scanchain>scan_vjtag.exe E:\Multiplier_4x3\TRACEFILE.txt out.txt
{'type': 6, 'id': 67330064, 'description': b'Dual RS232-HS A', 'serial': b'A'}

E:\Scanchain>
```

out.txt file generated after Scanchain testing:-

0000000 0000000 Success
0000001 0000000 Success
0000010 0000000 Success
0000011 0000000 Success
0000100 0000000 Success
0000101 0000000 Success
0000110 0000000 Success
0000111 0000000 Success
0001000 0000000 Success
0001001 0000001 Success
0001010 0000010 Success
0001011 0000011 Success
0001100 0000100 Success
0001101 0000101 Success
0001110 0000110 Success
0001111 0000111 Success
0010000 0000000 Success
0010001 0000010 Success
0010010 0000100 Success
0010011 0000110 Success
0010100 0001000 Success
0010101 0001010 Success
0010110 0001100 Success
0010111 0001110 Success
0011000 0000000 Success
0011001 0000011 Success
0011010 0000110 Success
0011011 0001001 Success
0011100 0001100 Success
0011101 0001111 Success
0011110 0010010 Success
0011111 0010101 Success
0100000 0000000 Success

0100001 0000100 Success
0100010 0001000 Success
0100011 0001100 Success
0100100 0010000 Success
0100101 0010100 Success
0100110 0011000 Success
0100111 0011100 Success
0101000 0000000 Success
0101001 0000101 Success
0101010 0001010 Success
0101011 0001111 Success
0101100 0010100 Success
0101101 0011001 Success
0101110 0011110 Success
0101111 0100011 Success
0110000 0000000 Success
0110001 0000110 Success
0110010 0001100 Success
0110011 0010010 Success
0110100 0011000 Success
0110101 0011110 Success
0110110 0100100 Success
0110111 0101010 Success
0111000 0000000 Success
0111001 0000111 Success
0111010 0001110 Success
0111011 0010101 Success
0111100 0011100 Success
0111101 0100011 Success
0111110 0101010 Success
0111111 0110001 Success
1000000 0000000 Success
1000001 0001000 Success
1000010 0010000 Success
1000011 0011000 Success

1000100 0100000 Success
1000101 0101000 Success
1000110 0110000 Success
1000111 0111000 Success
1001000 0000000 Success
1001001 0001001 Success
1001010 0010010 Success
1001011 0011011 Success
1001100 0100100 Success
1001101 0101101 Success
1001110 0110110 Success
1001111 0111111 Success
1010000 0000000 Success
1010001 0001010 Success
1010010 0010100 Success
1010011 0011110 Success
1010100 0101000 Success
1010101 0110010 Success
1010110 0111100 Success
1010111 1000110 Success
1011000 0000000 Success
1011001 0001011 Success
1011010 0010110 Success
1011011 0100001 Success
1011100 0101100 Success
1011101 0110111 Success
1011110 1000010 Success
1011111 1001101 Success
1100000 0000000 Success
1100001 0001100 Success
1100010 0011000 Success
1100011 0100100 Success
1100100 0110000 Success
1100101 0111100 Success
1100110 1001000 Success

1100111 1010100 Success
1101000 0000000 Success
1101001 0001101 Success
1101010 0011010 Success
1101011 0100111 Success
1101100 0110100 Success
1101101 1000001 Success
1101110 1001110 Success
1101111 1011011 Success
1110000 0000000 Success
1110001 0001110 Success
1110010 0011100 Success
1110011 0101010 Success
1110100 0111000 Success
1110101 1000110 Success
1110110 1010100 Success
1110111 1100010 Success
1111000 0000000 Success
1111001 0001111 Success
1111010 0011110 Success
1111011 0101101 Success
1111100 0111100 Success
1111101 1001011 Success
1111110 1011010 Success
1111111 1101001 Success